

CHECKING CIRCUITS FOR INTEGER MULTIPLICATION USING GRÖBNER BASES





Manuel Kauers · Institute for Algebra · JKU · Linz, Austria.


Joint work with Armin Biere and Daniela Ritirc

$$\underline{47495831406 \times 19167053557}$$
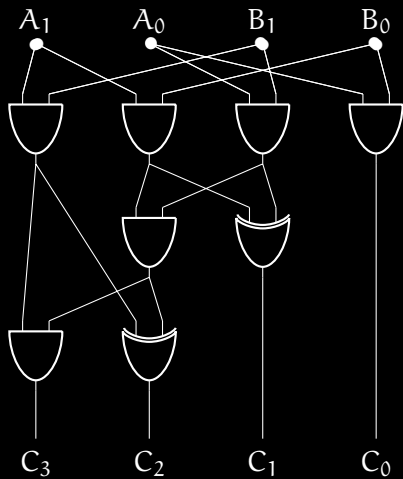
$$\underline{10001011001 \times 1101100001}$$



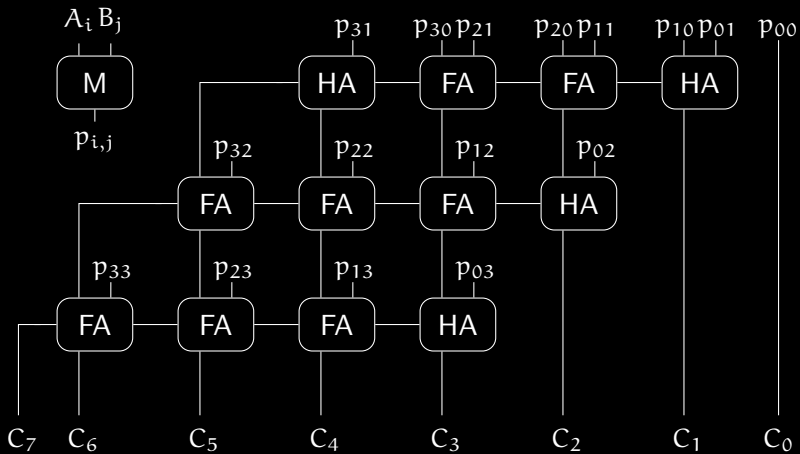

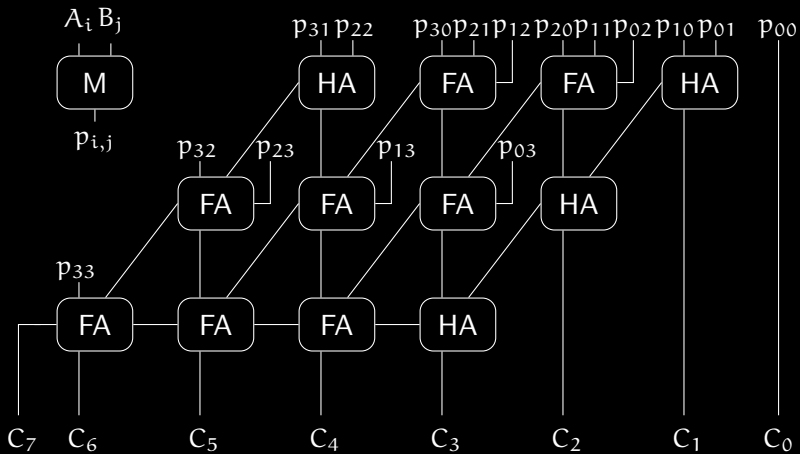

Questions:

Questions:

- Are these circuits correct?

Questions:

- Are these circuits correct?
- Are these circuits really correct?

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Yes, because we understand the idea and don't see any bug.

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Yes, because we proved its correctness by computer algebra.

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Yes, because we constructed a proof by computer algebra and checked it with a proof checker.

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

Questions:

- Are these circuits correct?
- Are these circuits really correct?
- Are these circuits really really correct?
- Are these circuits really really really correct?

Answers:

We don't know yet, because the proof checker we used is not formally verified.

Are they really correct?

- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$

- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$
- A circuit is “correct” if it corresponds the right function

- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$
- A circuit is “correct” if it corresponds the right function
- The behaviour of a gate is described by a polynomial equation

- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$
- A circuit is “correct” if it corresponds the right function
- The behaviour of a gate is described by a polynomial equation



- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$
- A circuit is “correct” if it corresponds the right function
- The behaviour of a gate is described by a polynomial equation



$$z = xy$$



$$z = x + y - 2xy$$

- Every circuit implements a certain function $\{0, 1\}^n \rightarrow \{0, 1\}^m$
- A circuit is “correct” if it corresponds the right function
- The behaviour of a gate is described by a polynomial equation



$$z = xy$$




$$z = x + y - 2xy$$




$$z = x + y - xy$$

- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




○ $C_0 = A_0B_0$

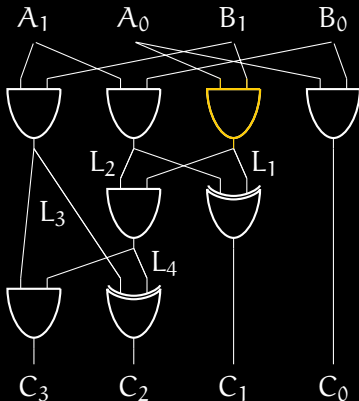- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$

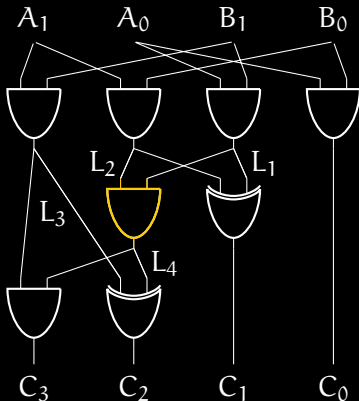- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$
- $L_4 = L_1L_2$

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.




- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$
- $L_4 = L_1L_2$
- $C_2 = L_3 + L_4 - 2L_3L_4$

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.



- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$
- $L_4 = L_1L_2$
- $C_2 = L_3 + L_4 - 2L_3L_4$
- $C_3 = L_3L_4$

 
- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.



- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$
- $L_4 = L_1L_2$
- $C_2 = L_3 + L_4 - 2L_3L_4$
- $C_3 = L_3L_4$

- We also have polynomials for restricting the range of the variables to $\{0, 1\}$.

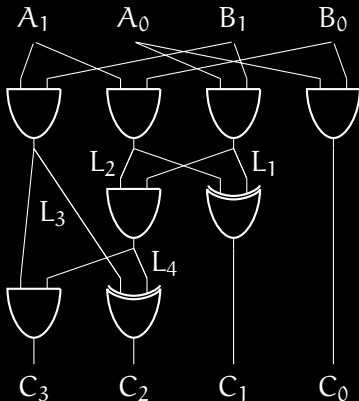
- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.



- $C_0 = A_0B_0$
- $L_1 = A_0B_1$
- $L_2 = A_1B_0$
- $L_3 = A_1B_1$
- $C_1 = L_1 + L_2 - 2L_1L_2$
- $L_4 = L_1L_2$
- $C_2 = L_3 + L_4 - 2L_3L_4$
- $C_3 = L_3L_4$
- $A_0(A_0 - 1) = 0$
- $A_1(A_1 - 1) = 0$
- $B_0(B_0 - 1) = 0$
- $B_1(B_1 - 1) = 0$

- We also have polynomials for restricting the range of the variables to $\{0, 1\}$.

 
- For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.



- $C_0 - A_0B_0 = 0$
- $L_1 - A_0B_1 = 0$
- $L_2 - A_1B_0 = 0$
- $L_3 - A_1B_1 = 0$
- $C_1 - L_1 - L_2 + 2L_1L_2 = 0$
- $L_4 - L_1L_2 = 0$
- $C_2 - L_3 - L_4 + 2L_3L_4 = 0$
- $C_3 - L_3L_4 = 0$
- $A_0(A_0 - 1) = 0$
- $A_1(A_1 - 1) = 0$
- $B_0(B_0 - 1) = 0$
- $B_1(B_1 - 1) = 0$

- We also have polynomials for restricting the range of the variables to $\{0, 1\}$.

 - For the whole circuit, we have one variable for each circuit input bit and each gate output, and one polynomial per gate.



- $C_0 - A_0B_0$
- $L_1 - A_0B_1$
- $L_2 - A_1B_0$
- $L_3 - A_1B_1$
- $C_1 - L_1 - L_2 + 2L_1L_2$
- $L_4 - L_1L_2$
- $C_2 - L_3 - L_4 + 2L_3L_4$
- $C_3 - L_3L_4$
- $A_0(A_0 - 1)$
- $A_1(A_1 - 1)$
- $B_0(B_0 - 1)$
- $B_1(B_1 - 1)$

- We also have polynomials for restricting the range of the variables to $\{0, 1\}$.

- The ideal generated by these polynomial contains all the polynomial relations implied by the circuit. The ideal is radical and has dimension zero.

- The ideal generated by these polynomial contains all the polynomial relations implied by the circuit. The ideal is radical and has dimension zero.
- The polynomials form a Gröbner bases for any lexicographic order such that $x_i < x_j$ whenever there is a gate that has x_i as input and x_j as output.

- The ideal generated by these polynomial contains all the polynomial relations implied by the circuit. The ideal is radical and has dimension zero.
- The polynomials form a Gröbner bases for any lexicographic order such that $x_i < x_j$ whenever there is a gate that has x_i as input and x_j as output.
- Taking \mathbb{Q} as ground field, a multiplier circuit is correct iff its ideal contains the polynomial

$$\left(\sum_{k=0}^{2^n-1} 2^k A_k \right) \left(\sum_{k=0}^{2^n-1} 2^k B_k \right) - \left(\sum_{k=0}^{2^{2n}-1} 2^k C_k \right)$$


- The ideal generated by these polynomial contains all the polynomial relations implied by the circuit. The ideal is radical and has dimension zero.
- The polynomials form a Gröbner bases for any lexicographic order such that $x_i < x_j$ whenever there is a gate that has x_i as input and x_j as output.
- Taking \mathbb{Q} as ground field, a multiplier circuit is correct iff its ideal contains the polynomial

$$\left(\sum_{k=0}^{2^n-1} 2^k A_k \right) \left(\sum_{k=0}^{2^n-1} 2^k B_k \right) - \left(\sum_{k=0}^{2^{2n}-1} 2^k C_k \right)$$


- Correctness thus reduces to ideal membership test.

If there is circuit which we know to be correct, we can also check whether another circuit implements the same function:

 If there is circuit which we know to be correct, we can also check whether another circuit implements the same function:



 If there is circuit which we know to be correct, we can also check whether another circuit implements the same function:



The circuits are equivalent iff $\sum_{k=0}^n 2^k (C_k - C'_k) \in I$.

- In theory, all this has been known for some time.

- In theory, all this has been known for some time.
- In practice, for nontrivial circuits, it's not as easy as it seems.

- **In theory**, all this has been known for some time.
- **In practice**, for nontrivial circuits, it's not as easy as it seems.
- As we get the Gröbner basis for free, we “just” have to compute a normal form.

- **In theory**, all this has been known for some time.
- **In practice**, for nontrivial circuits, it's not as easy as it seems.
- As we get the Gröbner basis for free, we “just” have to compute a normal form.
- For real world circuits (e.g., 64bit multipliers), this can be difficult.

- **In theory**, all this has been known for some time.
- **In practice**, for nontrivial circuits, it's not as easy as it seems.
- As we get the Gröbner basis for free, we “just” have to compute a normal form.
- For real world circuits (e.g., 64bit multipliers), this can be difficult.
- Some special purpose improvements we use in our code:
 - We divide the circuit into “slices” and do one reduction per slice. This prevents some bad choices during the reduction. [FMCAD'16]
 - We preprocess the Gröbner bases by eliminating some variables that only occur “locally”. This prevents some amount of expression swell. [DATE'18]

Are they really really correct?

- Can we trust the computer algebra system and/or the implementation of our own improvements?

- Can we trust the computer algebra system and/or the implementation of our own improvements?
- Can we construct a checkable **proof object** rather than a yes/no answer?

- Can we trust the computer algebra system and/or the implementation of our own improvements?
- Can we construct a checkable **proof object** rather than a yes/no answer?
- Recall: $g \in \langle f_1, \dots, f_m \rangle \iff g = p_1 f_1 + \dots + p_m f_m$ for certain polynomials p_i .

- Can we trust the computer algebra system and/or the implementation of our own improvements?
- Can we construct a checkable **proof object** rather than a yes/no answer?
- Recall: $g \in \langle f_1, \dots, f_m \rangle \iff g = p_1 f_1 + \dots + p_m f_m$ for certain polynomials p_i .
- These **cofactors** p_1, \dots, p_m can serve as certificate of the ideal membership.

- Can we trust the computer algebra system and/or the implementation of our own improvements?
- Can we construct a checkable **proof object** rather than a yes/no answer?
- Recall: $g \in \langle f_1, \dots, f_m \rangle \iff g = p_1 f_1 + \dots + p_m f_m$ for certain polynomials p_i .
- These **cofactors** p_1, \dots, p_m can serve as certificate of the ideal membership.
- Again, this is well-known in theory, but not so easy in practice: the cofactors can be quite large.

- Translate the defining properties of ideals into a formal proof system:

- Translate the defining properties of ideals into a formal proof system:

$$\forall p, q \in I : p + q \in I$$

- Translate the defining properties of ideals into a formal proof system:

$$\forall p, q \in I : p + q \in I$$

$$\forall p \in \mathbb{K}[X] \forall q \in I : pq \in I$$

- Translate the defining properties of ideals into a formal proof system:

$$\forall p, q \in I : p + q \in I \quad \rightsquigarrow \quad \frac{p \quad q}{p + q}$$

$$\forall p \in \mathbb{K}[X] \quad \forall q \in I : pq \in I \quad \rightsquigarrow \quad \frac{q}{pq}$$

- Translate the defining properties of ideals into a formal proof system:

$$\forall p, q \in I : p + q \in I \quad \rightsquigarrow \quad \frac{p \quad q}{p + q}$$

$$\forall p \in \mathbb{K}[X] \forall q \in I : pq \in I \quad \rightsquigarrow \quad \frac{q}{pq}$$

- We construct a formal proof by tracing the reduction process

$$\begin{array}{l} \vdots \\ * : -b+1-a, \quad a, \quad -a*b+a-a^2; \\ + : -a*b+a-a^2, \quad a^2-a, \quad -a*b; \\ + : -a*b, \quad -c+a*b, \quad -c; \\ * : -c, \quad -1, \quad c; \\ \vdots \end{array}$$

Observations: (for n -bit multipliers)

Observations: (for n -bit multipliers)

- Suppose that an ideal membership testing takes time X

Observations: (for n -bit multipliers)

- Suppose that an ideal membership testing takes time X
- Then proof generation costs $\approx 100X$

Observations: (for n -bit multipliers)

- Suppose that an ideal membership testing takes time X
- Then proof generation costs $\approx 100X$
- Verifying that the proof is correct costs $\approx X/100$

Observations: (for n -bit multipliers)

- Suppose that an ideal membership testing takes time X
- Then proof generation costs $\approx 100X$
- Verifying that the proof is correct costs $\approx X/100$
- Proof length seems to grow like $O(n^2)$

Observations: (for n -bit multipliers)

- Suppose that an ideal membership testing takes time X
- Then proof generation costs $\approx 100X$
- Verifying that the proof is correct costs $\approx X/100$
- Proof length seems to grow like $O(n^2)$
- Theoretical upper bound for resolution proof size $O(n^7 \log n)$
[Beame et al. 2017]

Are they really really really correct?

- Since the proof format is rather low-level, it doesn't take much to write a checker.

- Since the proof format is rather low-level, it doesn't take much to write a checker.
- We have written two checkers: one based on Python and Singular and another one purely in C.

- Since the proof format is rather low-level, it doesn't take much to write a checker.
- We have written two checkers: one based on Python and Singular and another one purely in C.
- But who will check the checkers? So far we have not made any efforts in this direction.

- Since the proof format is rather low-level, it doesn't take much to write a checker.
- We have written two checkers: one based on Python and Singular and another one purely in C.
- But who will check the checkers? So far we have not made any efforts in this direction.
- Also the script which turns the given circuit into polynomials might require verification.

- Since the proof format is rather low-level, it doesn't take much to write a checker.
- We have written two checkers: one based on Python and Singular and another one purely in C.
- But who will check the checkers? So far we have not made any efforts in this direction.
- Also the script which turns the given circuit into polynomials might require verification.
- No matter what we do: there is no absolute certainty, but we are reasonably sure that the circuits are correct.